

Aug 23rd - Report

Note Title

23-08-2012

ARM → Machine Insts. [ARCHITECTURE]

Basic Elements: [ORGANIZATION]

ALU: adder, shifter, multiplier
divider.

Memory: SRAM, DRAM, Flip-Flops

Adder

1 bit addition.

[HALF ADDER]

$$\begin{array}{r} c_1 \quad a_1 \\ + \quad b_1 \\ \hline S_1 \end{array}$$

$$S_1 = a_1 \oplus b_1$$

$$C_1 = a_1 \cdot b_1$$

\oplus \rightarrow exclusive or

\cdot \rightarrow and

Full Adder.

$$\begin{array}{r} C_1 \\ + \quad a_1 \quad \swarrow c_0 \\ \quad b_1 \\ \hline s_1 \end{array}$$

+ \rightarrow OR


$$s_1 = a_1 \oplus b_1 \oplus c_0$$

$$C_1 = a_1 \cdot b_1 + a_1 c_0 + b_1 c_0$$

n-bit addition

$$\begin{array}{r} a_n \quad \cdot \quad \cdot \quad \cdot \quad \cdot \quad a_1 \\ + \quad b_n \quad \cdot \quad \cdot \quad \cdot \quad \cdot \quad b_1 \\ \hline C_n \quad s_n \quad \cdot \quad \cdot \quad \cdot \quad \cdot \quad s_1 \\ \hline n+1 \end{array}$$

Ripple Carry Adder.

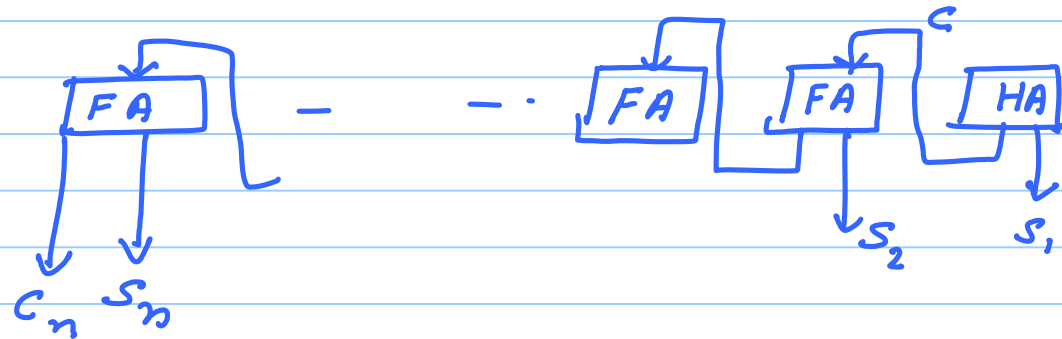

Carry is rippling from the first to last adder


Time it takes to do addition : $O(n)$
[slow]

Reason for slow operation:

position 1 n The carry is propagating from

Carry - Select Adder
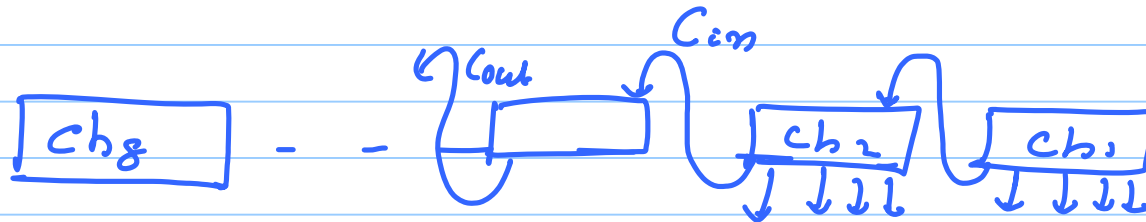
$$\begin{array}{ccccccc}
 & & \text{chunk 8} & & \text{chunk 7} & & \text{chunk 1} \\
 & & [a_{32} \dots a_{29}] & [a_{28} \dots] & - & - & [a_4 a_3 a_2 a_1] \\
 + & & [b_{32} \dots b_{29}] & [b_{28} \dots] & - & - & [b_4 b_3 b_2 b_1] \\
 \hline
 c_{32} & s_{32} & - & - & - & - & s_1
 \end{array}$$



Carry Select Adder.

Stage 1:

forall chunks,

compute two results


result₁ (assuming $C_{in} = 1$)
(sum bits &
 C_{out})
result₀ (assuming $C_{in} = 0$)

Chunk size is k

Time (Stage₁) : $O(k)$

Stage 2:

Make the carry ripple across chunks

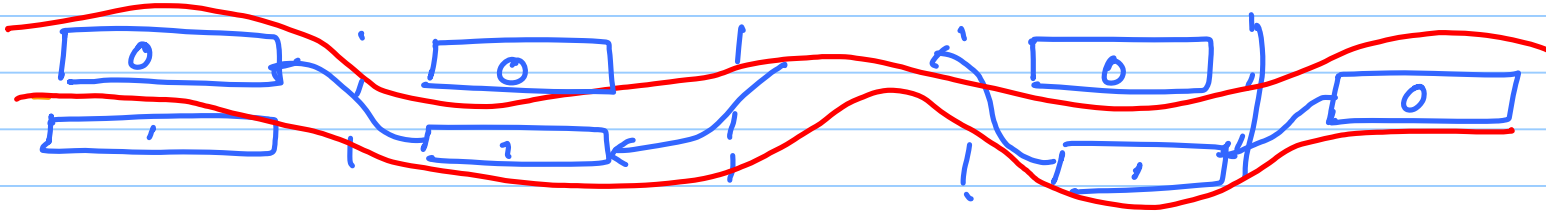

Time (Stage₂) = #chunks: n/k

$$\text{Time: } \left\{ k + \frac{n}{k} \right\}$$

E.g. 8 bit addition chunk size is 2

$$\begin{array}{cccc} C_4 & C_3 & C_2 & C_1 \\ 10 & 11 & 00 & 01 \\ 11 & 01 & 00 & 11 \\ \hline \end{array}$$

Stage 1

$$\begin{array}{cccc} C_4 & C_3 & C_2 & C_1 \\ \hline 101 & 100 & 000 & 100 \\ 110 & 101 & 001 & \uparrow \text{Sum} \\ & & & c \end{array}$$

Stage 2

$$\begin{array}{cccc} C_{in} = 0 & 101 & \underline{100} & 000 \\ C_{in} = 1 & \underline{110} & 101 & \underline{001} \end{array}$$

| 10 00 01 00 ✓

Time: $k + n/k$

$$f(k) = k + \frac{n}{k}$$

$$\frac{df(k)}{dk} = 1 - \frac{n}{k^2} = 0$$

$$\Rightarrow k = \sqrt{n}$$

optimal chunk size:
 \sqrt{n}

Time: $2\sqrt{n} \leftrightarrow O(\sqrt{n})$

Extension

Time waste:

A unit (chunk) is idle in the

2nd stage after it has done its job.

variable sized chunk.



$$\sum_{i=1}^m i = n$$

Operation:

1) Every chunk computes two results ($C_{in} = 0$, $C_{in} = 1$)

2) Claim:

The moment it is done with its computation it gets the right value of C_{in}

Proof

Mathematical Induction

Base Case: chunk₁
Con = 0 ✓

Induction Case:
ith Chunk

At time (i) → finishes its computation.

By induction hypothesis, the previous chunk

finishes its computation in time (i-1) and forwards the correct Con to chunk i by

time i.
→ Before time (i+1), compute the right value of Con for chunk (i+1) □

Total time: $O(m)$

$$\sum_{i=1}^m i = n$$

$$\Rightarrow \frac{m(m+1)}{2} = n$$

$$\Rightarrow m^2 + m - 2n = 0$$

$$m = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{-1 \pm \sqrt{1 + 8n}}{2}$$

$$m = \frac{\sqrt{8n+1} - 1}{2}$$

$$= \sqrt{2n + 1/4} - 1/2 \approx \sqrt{2} \cdot \sqrt{n}$$

Time: $O(m) = O(\sqrt{n})$ (complexity is same as fixed chunk algo.)

Time:

Algorithm	Exact Time	Asymptotic Time
1) Ripple Carry Adder	$\approx n$	$O(n)$
2) Carry Select Adder (Fixed size chunks)	$\approx 2\sqrt{n}$	$O(\sqrt{n})$
3) Carry Select Adder (Variable size chunks)	$\approx \sqrt{2} \cdot \sqrt{n}$	$O(\sqrt{n})$
4) Carry Lookahead Adder	$\approx 2 \cdot \log(n)$	$O(\log(n))$

Carry Lookahead Adder

$$\begin{array}{r} 0 \leftarrow C_{in} \\ + 0 \\ \hline 0 \\ C_{out} = 0 \\ \text{[absorb]} \end{array}$$

$$\begin{array}{r} 0 \leftarrow C_{in} \\ + 1 \\ \hline 1 \\ C_{out} = 1 \\ C_{out} = C_{in} \\ \text{[propagate]} \end{array}$$

$$\begin{array}{r} 1 \leftarrow C_{in} \\ + 1 \\ \hline 0 \\ C_{out} = 1 \\ \text{[generate?]} \end{array}$$

$$\begin{array}{r} a_1 \\ + b_1 \\ \hline \dots \end{array}$$

$$G_1 = a_1 \cdot b_1 \\ \text{(generate)}$$

$$P_1 = a_1 \oplus b_1 \\ \text{(propagate)}$$

$$+ \begin{array}{r} a_2 \quad a_1 \\ b_2 \quad b_1 \\ \hline \end{array}$$




$$C_{out} = G + P \cdot C_{in}$$

For a 1-bit chunk:

we have equations for G and P

Multi Bit System.

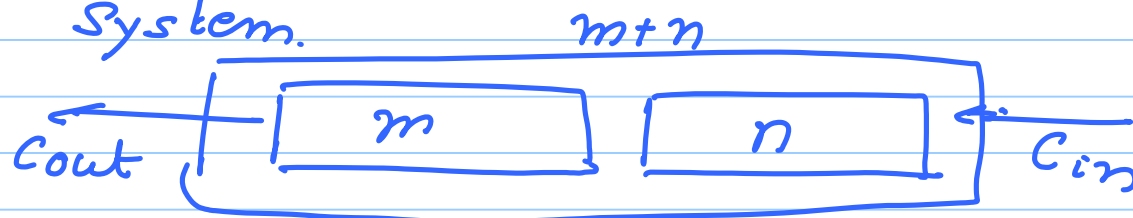

$$G_{m+n} = G_m + P_m \cdot C_n$$

$$P_{m+n} = P_m \cdot P_n$$

(1)

E.g.

$$\begin{bmatrix} a_2 & a_1 \\ b_2 & b_1 \end{bmatrix}$$

$$\begin{array}{r} \\ \\ + \\ \hline \textcircled{1} \\ \\ \\ \hline \textcircled{1} \end{array}$$

$$G = a_2 \cdot b_2 + (a_2 \oplus b_2) \cdot a_1 \cdot b_1$$
$$P = (a_1 \oplus b_1) \cdot (a_2 \oplus b_2)$$

$$G_1 = a_1 \cdot b_1 \quad P_1 = a_1 \oplus b_1$$

$$G_2 = a_2 \cdot b_2 \quad P_2 = a_2 \oplus b_2$$

$$\begin{cases} G = G_2 + P_2 \cdot G_1 \\ P = P_2 \cdot P_1 \end{cases} \quad \dots (2)$$

 TODO: Go to the web and understand this

Tutorial This week: Sunday (10 - 1 pm)

Tomorrow

Carry Lookahead Adder.